

## Part C

Answer any **one** full questions from each module.  
Each full question carries 12 marks.

## MODULE I

11. Find  $v_L$  in the circuit of Fig. 1 using Superposition theorem.

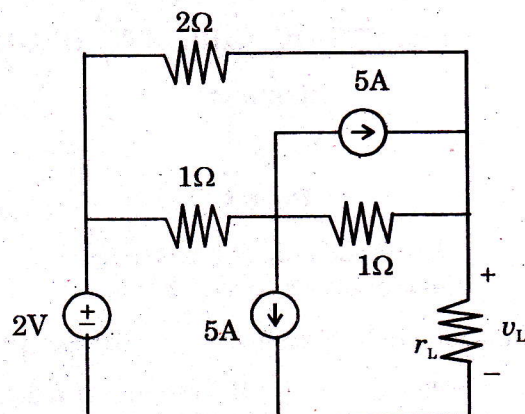


Fig. 1

Or

12. Obtain the maximum amount of power transfer in  $R$  from the sources using the theorems of Maximum power transfer in the network shown in Fig. 2. At what value of  $R$  the maximum power transfer will occur?

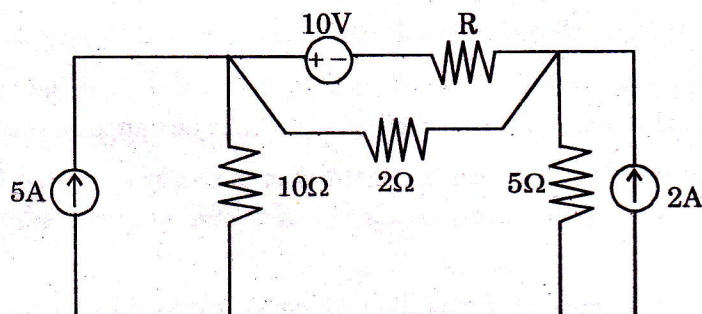


Fig. 2

## MODULE II

13. An a.c. voltage of  $v = V \sin 500 \pi t$  is applied to a series RL circuit. If the  $L - R$  circuit has  $R = 10 \Omega$  and  $L = 0.1 \text{ H}$ , calculate the ratio of maximum value to which the current rise to the steady state maximum value when the voltage is applied at an instant  $t = 0.002 \text{ sec}$ .

Or