

MODULE IV

17. In the circuit shown in Fig. 6, find the voltage across the 10 ohm resistor and also the current supplied by the source :

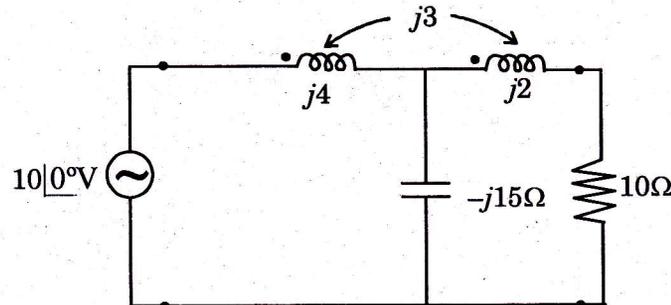


Fig. 6

Or

18. Synthesise the following driving point impedance in both the foster forms and draw the network.

(a)
$$\frac{s(s^2 + 2)(s^2 + 5)}{(s^2 + 1)(s^2 + 4)}$$

(b)
$$\frac{(s^2 + 2)(s^2 + 5)}{s(s^2 + 4)(s^2 + 9)}$$

MODULE V

19. Between any two terminals of a 3-phase balanced load the voltage is 415 volt and the resistance is 3 Ω. The current in each of the lines is 100 A and the supply phase sequence is RYB. Find the power factor of the load. Find also the resistance and reactance per phase of the load with :

(i) Star Connection.

(ii) Delta Connection.

Or

20. A 3-phase, 440 V delta connected system has the loads : branch RY, 20 kW at unity power factor ; branch YB, 30 kVA at power factor 0.8 lagging ; branch BR , 20 kVA at power factor 0.6 leading. Find (a) the line currents ; and (b) balanced Y connected resistors that would take same power as the above load from the same supply.

(5 × 12 = 60 marks)